
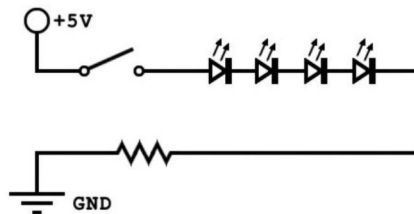
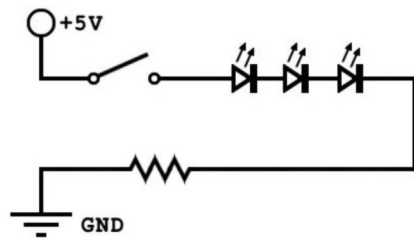
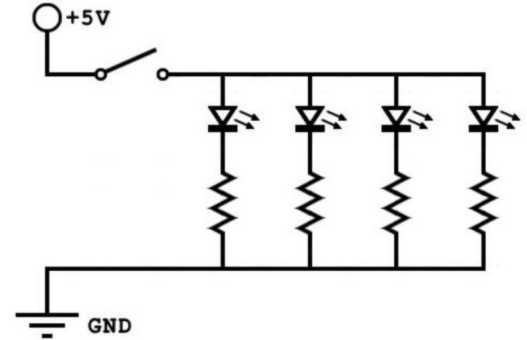
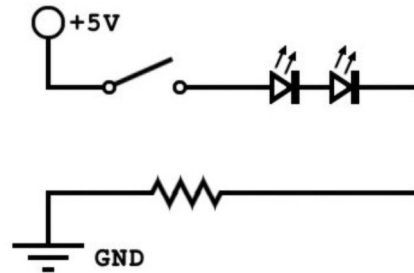
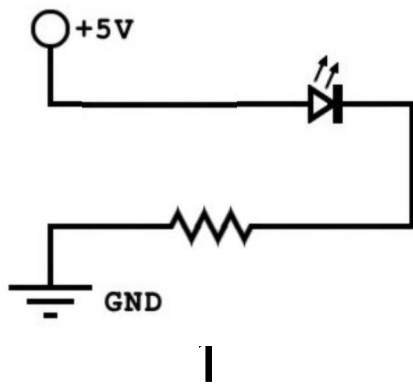


SERIES & PARALLEL

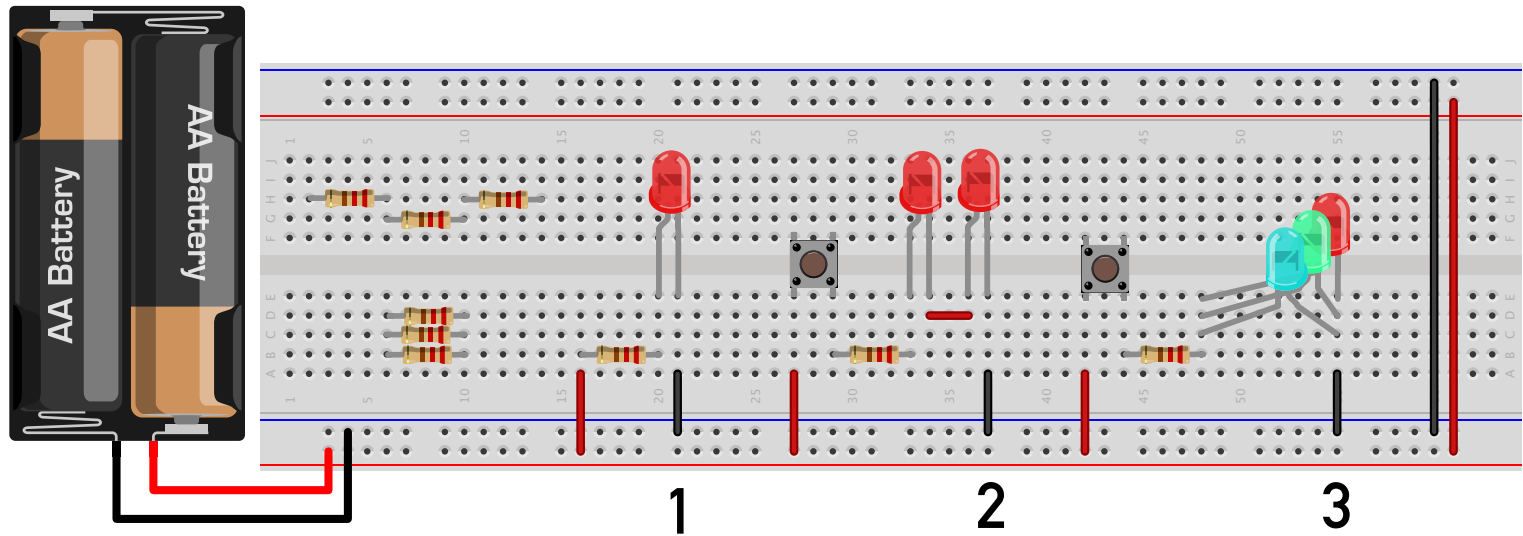

2

integrated circuit:

IC1: 555 timer

 notch goes to the left
 pins numbered CCW from bottom left pin

resistors:

R1: 10K (brown-black-orange)
 R2: 100K (brown-black-yellow)
 R3: 1K (brown-black-red)



capacitor:

C1: 10uF electrolytic

 stripe indicates negative leg

LED:

LED1: light emitting diode

 bottom view:
 flat side is negative leg