
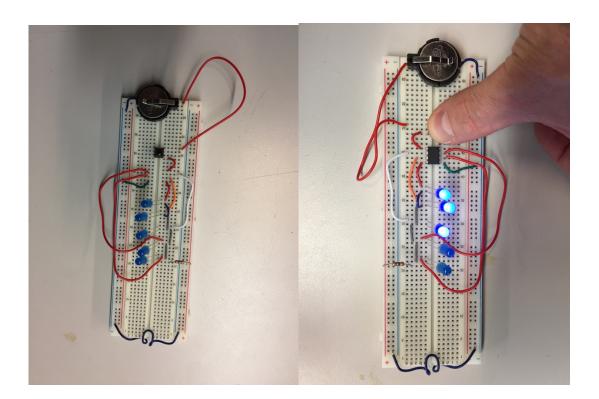
A) My strategy was to put together the bread board first to see make sure that power was flowing from the battery to all the LED lights.



Then I uploaded the code of Elio into the microcontroller to see how that worked once in the bread board. After which I looked at the code to figure out how my chosen work "BINGO" is set up in the LED lights. Had I not asked about the grid on which they are created I would never have known where they came from. This allowed me to add a smiley face at the end.

PM 8 = Nomertary Switch	6= {31, 21, 21, 10,0} i= {0,17,31,17,0}
LED 1 = Pm 5	
LED 2 = PIN 6	0 0 0 0 0 0 0 -
CED 3 = Pm 7 or 3	N= \{31, 12, 3, 31, 0} &= \{14, 17, 19, 10, 0\}
LED 4 = Pin 3 Resistor grounds	0 0
LED 5 = Pin 2	0 - 0 - 0 - 0 - 0 -
Ground to- Pm 4 battery	0 + 0 - 0 0 0 -
Pull y	0={14,17,17,14,0}
	- 6
	0 0 - 0 0

After this I uploaded the new code into the microcontroller and began doing the set up for my circuit board. I found the soldering particularly challenging and had to start over as I was using too much lead solder. Part way through Elio noticed my battery holder was put in backwards, which reversed the flow of power, so I had to put the actual battery in upside down to get the power going to pin 4. In the end I managed, and miraculously got it done and working after the first go. Phew! I can't say my soldering job was elegant but not bad for a first project.

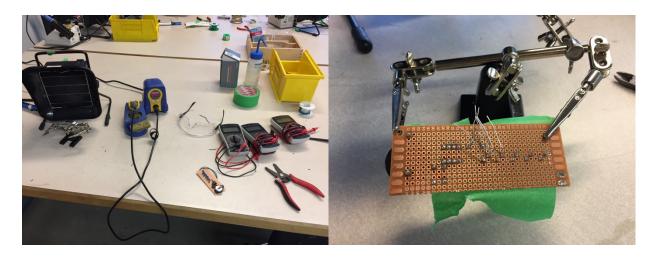

Getting the image to actually appear with some legibility was not so easy but you can kind of see it is there.

